

CONCEPT 2010





Targets of the Basic Boards for 2SC0435T and 2SC0108T

- Support of our customers when using 2SC0108T and 2SC0435T
- Schematics and Layout available on www.IGBT-Driver.com
- User can reuse the schematics and merge it in it own circuit
- User can buy the basic board as a complete solution by CONCEPT sales partner
- User can produce the basic board on its own
- → "Plug-and-play" drivers for 34mm (2SC0108T) and 62mm (2SC0435T) IGBT modules
- → "Plug-and-play" drivers for 600V, 1200V and 1700V IGBTs
- Use of CONCEPT DIC-20 standard interface

- Schematics / Gerber files will be available soon
- → Samples and high volume will also be provided to our customers soon



Agenda

2BB0435T2A0-XX Basic Boards for 2SC0435T

- Layout
- Schematics Overview
- Detailed Functionality
- Layout
- Direct Paralleling

2BB0108T2A0-XX Basic Boards for 2SC0108T and General Information


- Layout
- Schematics Overview
- Direct Paralelling

General Information

Don'ts from our Experience




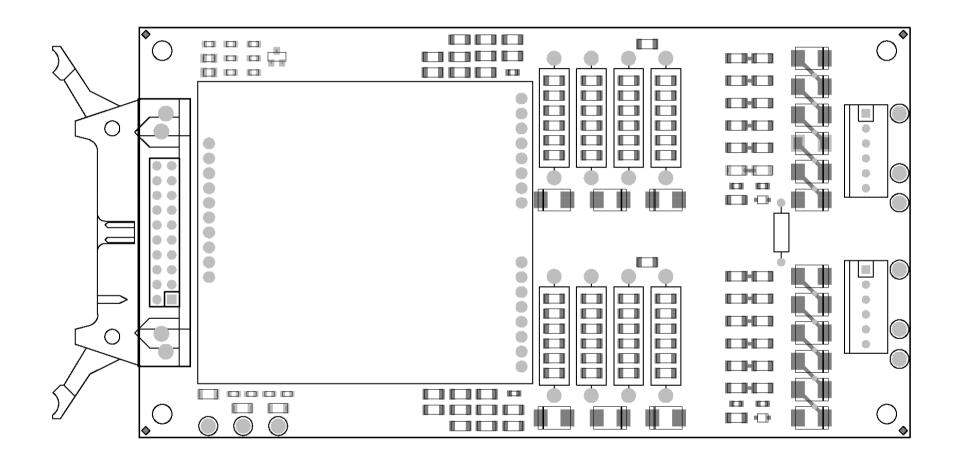Basic Board Layout 2BB0435T2A0-XX for 2SC0435T






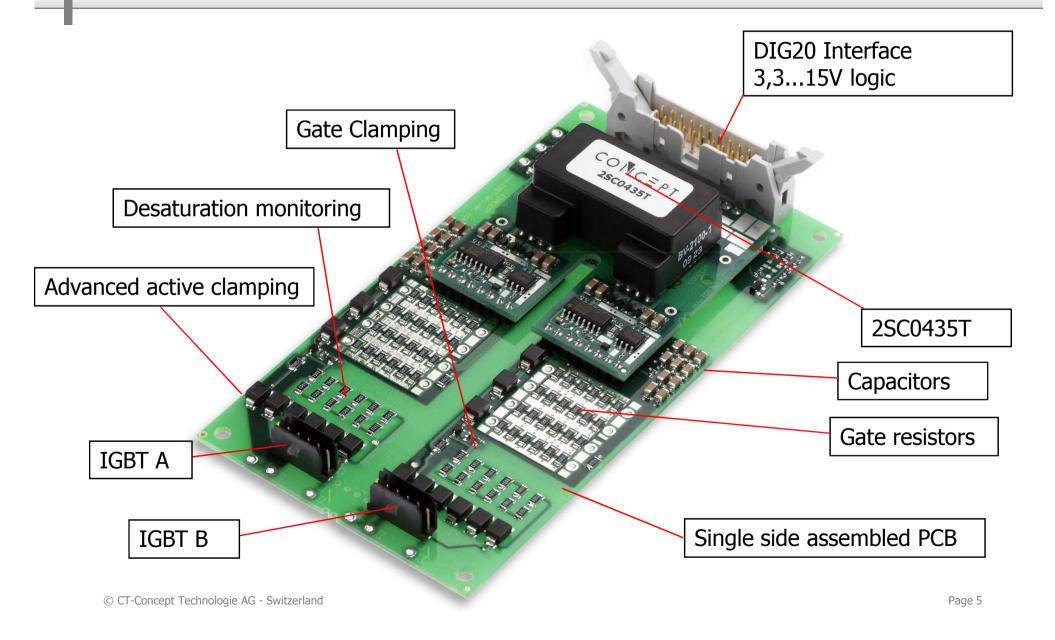Overview of Basic Board based 2BB0435T2A0-XX for 2SC0435T





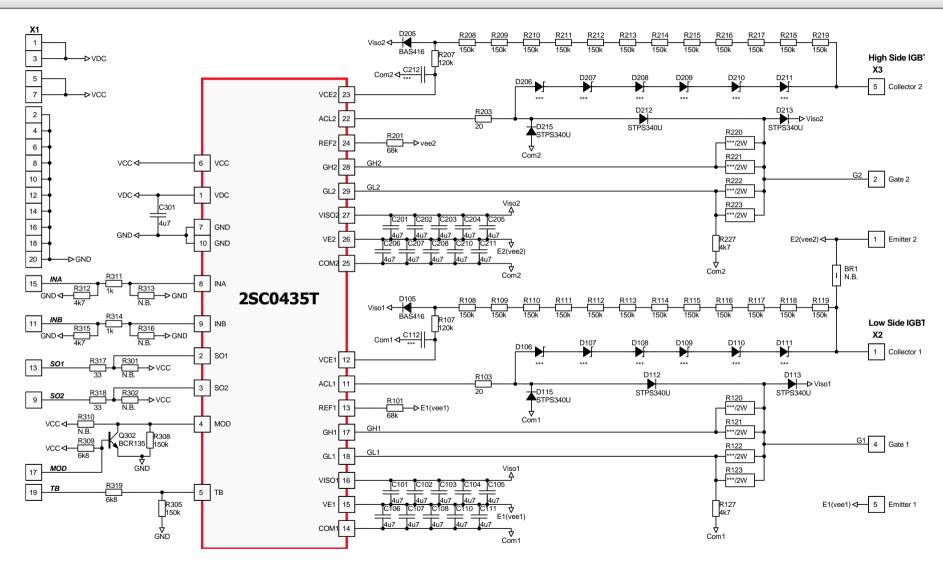Schematics Overview of Basic Board based on 2SC0435T





Primary Side Connector – Standard DIC20 Electrical Interface

| | _ | |
|----------------|---|----|
| Pin | | D |
| 1,3 | | V |
| 5,7 | | ٧ |
| 9 | | S |
| 11 | | II |
| 13 | | S |
| 15 | | II |
| 17 | | M |
| 19 | | Т |
| | | |
| 2,4,6,8,10, | | |
| 12,14,16,18,20 | | G |


| Des. |
|------|
| VDC |
| VCC |
| SO2 |
| INB |
| SO1 |
| INA |
| MOD |
| ТВ |
| |
| |
| GND |

| Function | |
|-------------------------------------|--|
| +15V for DC/DC converter | |
| +15V for primary side electronics | |
| Status output channel 2 | |
| Signal input B | |
| Status output channel 1 | |
| Signal input A | |
| Mode selection (direct/half-bridge) | |
| Blocking time | |
| | |
| | |
| Ground | |



Primary Side Connector – Supply Voltage VDC and VCC

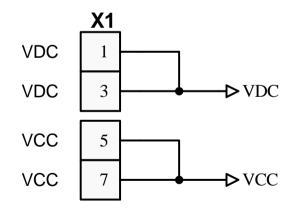
- Supply voltage of primary side electronics and DC/DC converter are available as separate pins for testing purposes
- Only one +15V supply voltage is required
- The driver limits the inrush current at startup, no external current limitation of the voltage source for VDC is needed.






Primary Side Connector – MOD Pin

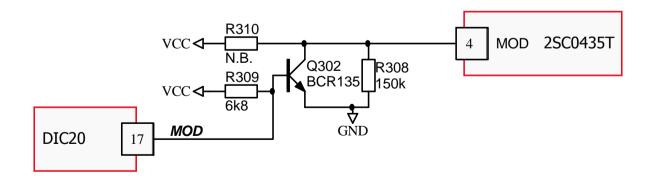- Allows to select direct mode or half-bridge mode
- Direct mode: MOD not connected (open) or connected to VCC INA drives channel 1, INB drives channel 2
- Half-bridge mode: MOD connected to GND
 See exact functionality on next page
 Dead time predefined with R303=150k → 3us
 Selectable dead time range: 0.6us 4.1us






Primary Side Connector – MOD Pin

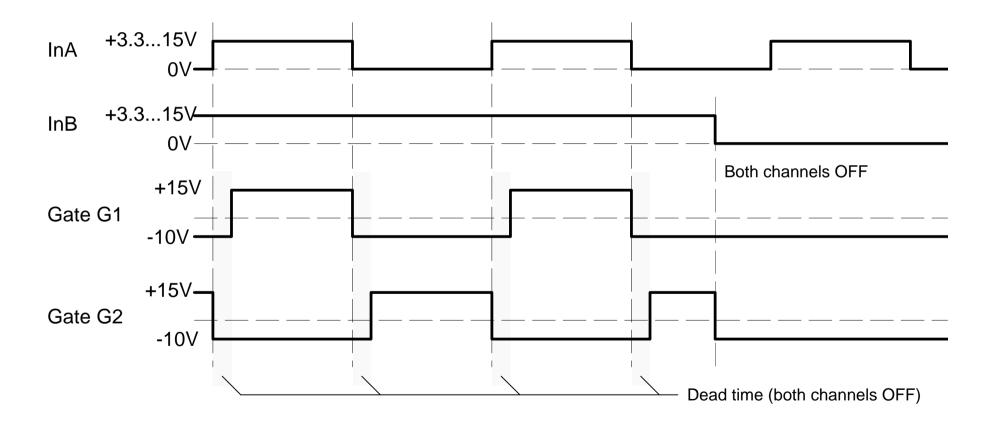



Primary Side Connector – Input Signals INA and INB

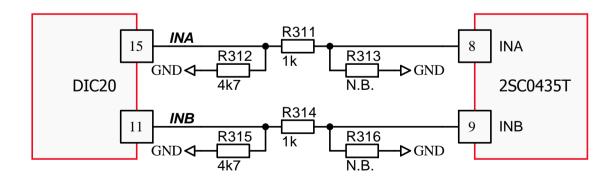
- INA and INB are drive inputs (Functionality: see MOD pin)
- Input hysteresis: 2.6V (turn-on), 1.3V (turn-off)
- Input hysteresis can be increased thanks to R313 and R316
- Accepted logic level: 3.3V 15V
- Caution: high slew rates (>0.25V/ns) are required in order to get small jitter values (~ 2-3ns)





Primary Side Connector – Blocking Time

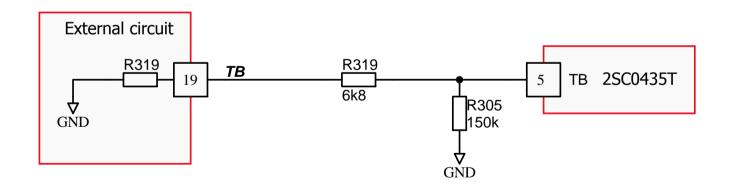
- Blocking time:
 - Corresponding channel is blocked (IGBT is turned off)
 - Corresponding status output (SOx) is connected to GND
- Predefined blocking time: 90ms, adjustable to 9us or 20ms-90ms with an external resistor (R319)





Primary Side Connector – Status Outputs SO1 and SO2

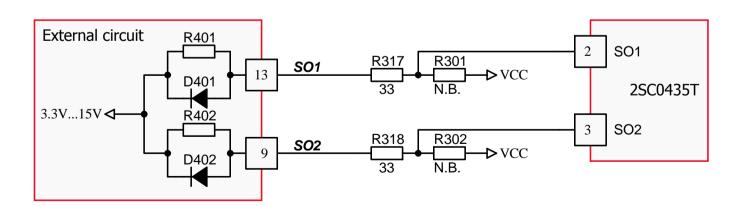
- No fault: SOx are at ~4V without external pull-up or VCC with pull-up resistors
- Fault on SOx:
 - Primary supply undervoltage: SO1 and SO2 are connected to GND
 - Secondary supply undervoltage or IGBT short-circuit: SO1 and SO2 are connected to GND during the blocking time
- Max. SOx current: 20mA
- Internal (R301/R302) or external (R401/R402) pull-up resistors can be used





Secondary Side Interface – Gate Outputs GLx and GHx

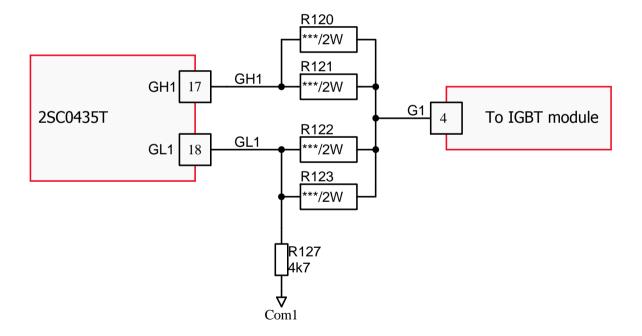
- Use of separated turn-on and turn-off resistors (no additional diode is required)
- Separated turn-on and turn-off gate resistors are required!





Secondary Side Interface – DC/DC Output (VISOx, VEx and COMx)

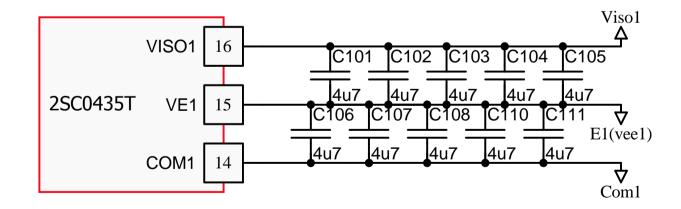
- Additional capacitors are used on the driver secondary side
- Recommended capacitors and capacitance:
 - Ceramic capacitors (> 25V)
 - 3uF capacitance per 1uC gate charge between VISOx-VEx and VEx-COMx
- No static load must be applied between VISOx-VEx or VEx-COMx





Secondary Side Interface – Desaturation Protection

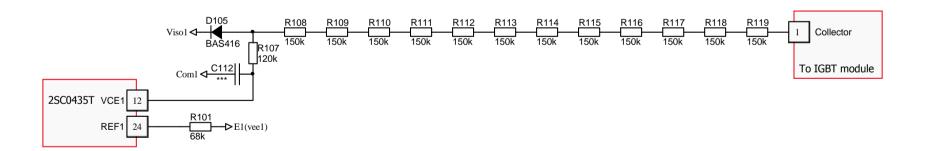
- ▶ Detection level pre-programmed at 10.2V with Rx01=68k
- Response time pre-programmed with capacitor Cx12
- ▶ Diode Cx05 must be low-leakage diodes (e.g. BAS416). Schottky diodes must be explicitly avoided





Secondary Side Interface – Advanced Active Clamping

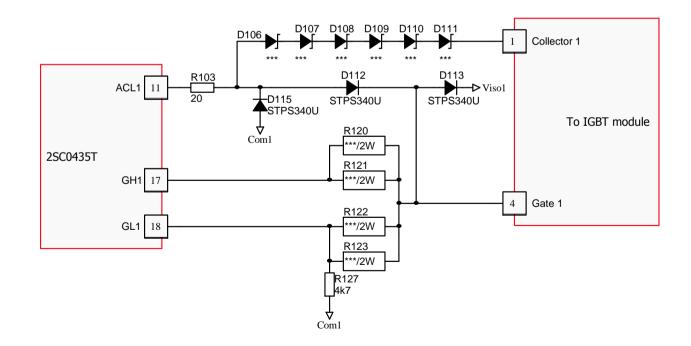
- Overvoltage protection at turn-off
- Collector feedback to the gate (basic AC) and to the driver (advanced AC)
 - More efficient collector-emitter voltage reduction
 - Less losses through the clamping devices (transient voltage suppressors)





Parallel Connection of SCALE-2 Basic Boards

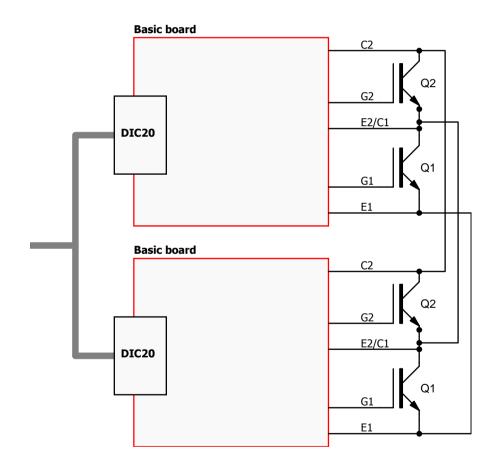- SCALE-2 technology provide direct paralleling function.
- The basic board with its own IGBT module can be directly parallel connected (direct paralleling)
- Advantages are galvanic insulated gate loops.
- Consult application note
 AN-0904 for more information





Agenda

2BB0435T2A0-XX Basic Boards for 2SC0435T

- Layout
- Schematics Overview
- Detailed Functionality
- Layout
- Direct Paralleling

2BB0108T2A0-XX Basic Boards for 2SC0108T and General Information


- Layout
- Schematics Overview
- Direct Paralelling

General Information

Don'ts from our Experience




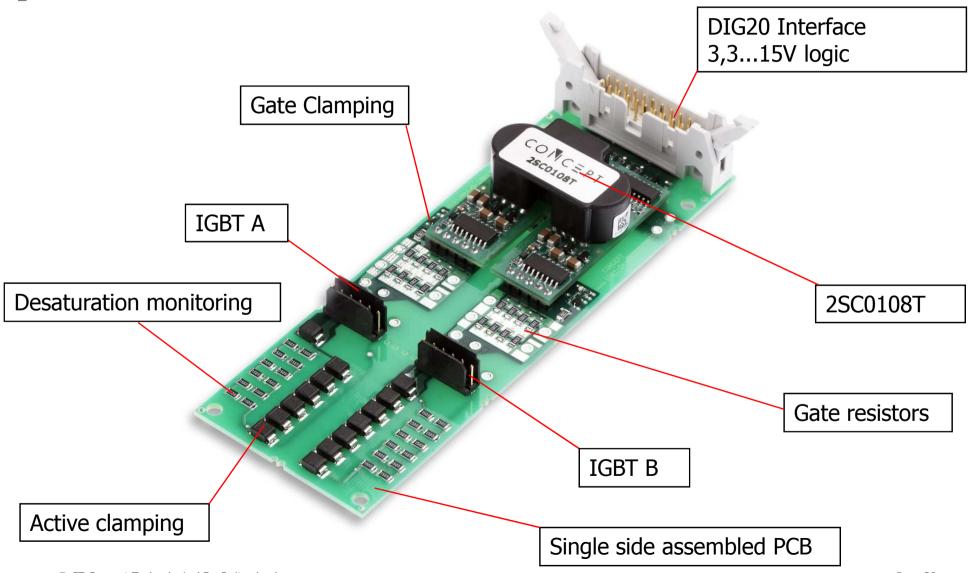Overview of Basic Board 2BB0108T2A0-XX for 2SC0108T





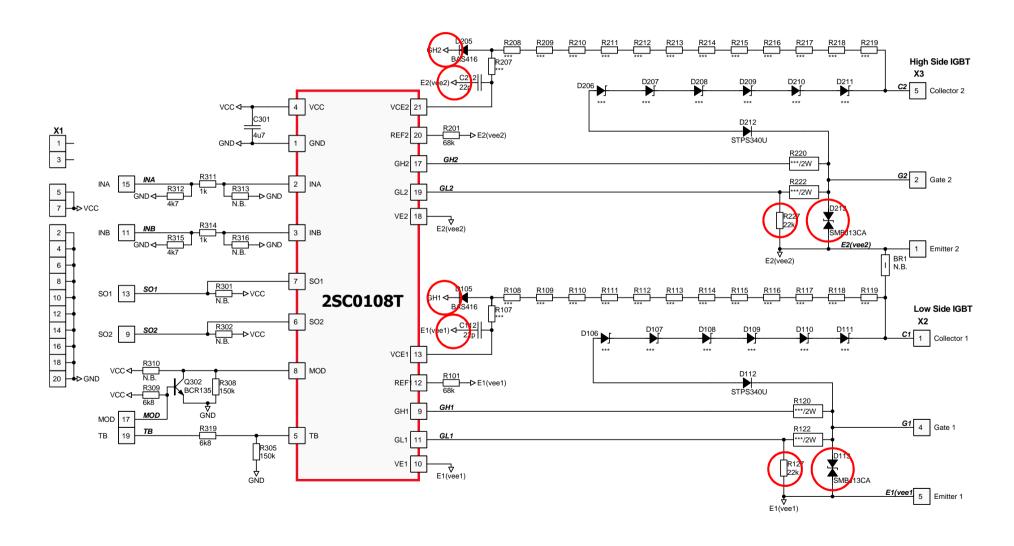Schematics Overview of Basic Board based on 2SC0108T






Parallel Connection of Basic Boards

- The basic board with its own IGBT module can be directly parallel connected (direct paralleling)
- Consult application note

 AN-0904 for more information

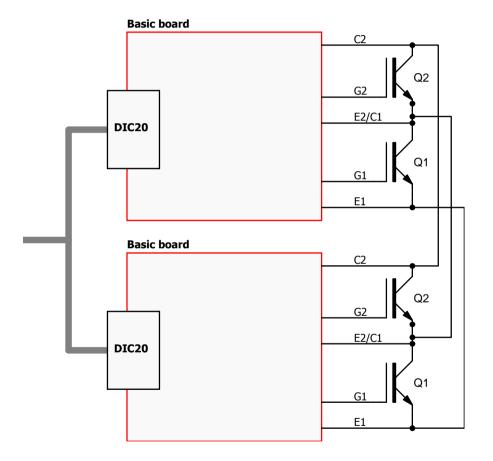



Agenda

2BB0435T2A0-XX Basic Boards for 2SC0435T

- Layout
- Schematics Overview
- Detailed Functionality
- Layout
- Direct Paralleling

2BB0108T2A0-XX Basic Boards for 2SC0108T and General Information

- Layout
- Schematics Overview
- Direct Paralelling


General Information

Don'ts from our Experience




Summary of Don'ts using 2SC0108T and 2SC0435T

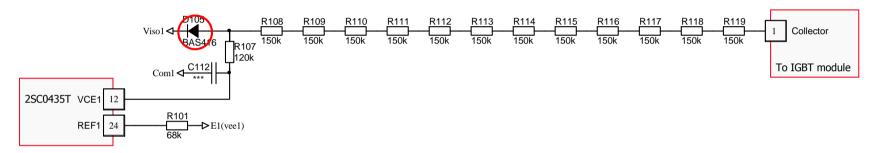■ Don't replace low-leakage diodes (where specified) with Schottky diodes!!



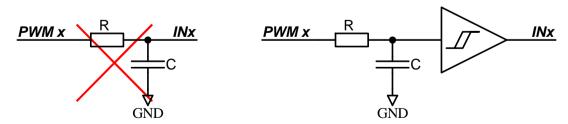▶ Don't Filter the input signals INA and INB (high increase of jitter)
 → If short-pulse suppression is required, the input signals to INA and INB can be filtered. A Schmitt-Trigger buffer must however be placed between filter and INA/INB!






Summary of Don'ts using 2SC0108T and 2SC0435T

▶ Don't short-circuit GLx and GHx and use one common gate resistor



Don't place static loads between VISOx-VEx or VEx-COMx, but between VISOx-

COMx

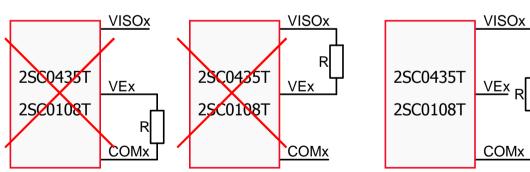

- Don't set low reference voltages for desaturation protection (recommendation)
 - → Desaturation monitoring is intended for short-circuit, not for accurate overcurrent protection



Many Thanks!

